

Tutorial Sheet -0.2.

Q1

$$\text{Rating} = 100 \text{ kVA}$$

$$V_1 = 4000 \text{ V}$$

$$V_2 = 200 \text{ V}$$

$$f_2 = 50 \text{ Hz}$$

$$N_2 = 100$$

$$(a) I_1, I_2 = ?$$

$$(b) N_1 = ?$$

$$(c) \phi_m = ?$$

(a)

$$I_1 = \frac{V_2}{V_1} \times 100 \text{ A} = \frac{200}{4000} \times 100 \text{ A} = 0.05 \text{ A} = 50 \text{ mA}$$

$$= \frac{100 \times 1000}{400} = 250 \text{ A} = 0.25 \text{ A}$$

$$= 25 \text{ A}$$

~~I₁~~

$$I_2 = \frac{V_1}{V_2}$$

$$= \frac{4000 \times 1000}{200} = 20000 \text{ A}$$

$$= 200 \text{ A}$$

(b)

$$\frac{V_2}{V_1} = \frac{N_2}{N_1}$$

$$\text{or } N_1 = \frac{V_1 \times N_2}{V_2}$$

$$= 2000$$

(c) from emf equation of primary side

$$\frac{N_1}{4.44} \times 900 \text{ of } N_1 \text{ per} \\ \text{amp}^2 = 9.01 \text{ mwp}$$

$$\frac{N_1}{4.44} \times \frac{V_1}{N_1} = 9.01 \text{ mwp}$$

\therefore

$$Z_1 = 14,400 \Omega$$

$$Z_2 = 400 \Omega$$

turns ratio

$$\frac{N_1}{N_2} = ?$$

$$Z_1 = \frac{Z_2}{k^2} = Z_2$$

$$k^2 = \left(\frac{N_2}{N_1}\right)^2$$

$$= \left(\frac{N_1}{N_2}\right)^2 \cdot Z_2$$

$$\left(\frac{N_1}{N_2}\right)^2 = \frac{Z_1}{Z_2}$$

or

$$\frac{N_1}{N_2} = \left(\frac{Z_1}{Z_2}\right)^{1/2}$$

$$= 6$$

$$\text{So, } \boxed{N_1 : N_2 = 6 : 1}$$

\therefore

$$\frac{N_1}{N_2} = \frac{5}{1}$$

$$+ Z_2 = 900 \Omega$$

$$\left(\frac{Z_1}{Z_2}\right)^2 = \left(\frac{N_1}{N_2}\right)^2$$

(a)

$$Z_1 = \left(\frac{5}{1}\right)^2 \times 900$$

$$= 22,500 \Omega$$

(b)

$$V_1 = 4500 V$$

$$V_2 = 225 V$$

$$f = 50 Hz$$

$$\frac{E}{N} = 15 V$$

$$B_m = 1.04 T$$

$$(a) N_1, N_2 = ?$$

$$(b) a = ?$$

$$\frac{V_2}{V_1} = \frac{E_2}{E_1} = \frac{N_2}{N_1}$$

$$\frac{E_2}{N_2} = \frac{E_1}{N_1} = 15$$

let $E_2 = V_2, E_1 = V_1$

$$\text{So, } \frac{V_2}{N_2} = 15$$

$$N_2 = \frac{V_2}{15}$$

Similarly,

$$\frac{V_1}{N_1} = 15$$

N_1

$$\text{or } N_1 = \frac{V_1}{15} = 300$$

(b) from CMF equation,

$$V_1 = 4.44 \varphi m / N_1$$

$$\varphi m = \frac{V_1}{4.44 N_1} = 0.0675$$

$$B_m = \varphi m$$

$$\text{or } a = \varphi m = 0.0675$$

$$\therefore A = \frac{\varphi m}{\varphi m} = 0.0675$$

$$\therefore A = 0.048 \text{ m}^2$$

$$V_1 = 110V, V_2 = 11V$$

$$N_2 = 20, N_1 = ?$$

$$\frac{V_2}{V_1} = \frac{N_2}{N_1}$$

$$\therefore N_1 = \frac{V_1}{V_2} \times N_2$$

$$\therefore \frac{110}{11} \times 20 = 200$$

$$\frac{V_2'}{V_2} = \frac{N_2'}{N_1}$$

$$N_2' = \frac{V_2'}{V_1} \times N_1$$

$$\therefore \frac{85}{110} \times 200$$

$$\therefore N_2' = 60.$$

No. of extra turns

$$\therefore N_2' - N_2$$

$$\therefore 60 - 20 = \boxed{40}$$



Page No.:

Date:

Q1

$$V_1 = 2400 \text{ V}$$

$$V_2 = 400 \text{ V}$$

$$I_0 = 0.5 \text{ A}$$

$$P_C = 400 \text{ W}$$

$$I_m^*, I_C = ?$$

we know that at no-load condition.

$$P_C = V_1 I_0 \cos \phi_0$$

$$\text{a) } \cos \phi_0 = \frac{P_C}{V_1 I_0} = \frac{400}{2400 \times 0.5} = 0.33$$

So,

$$\text{b) } I_0 = \frac{P_C}{V_1 \cos \phi_0} = \frac{400}{2400 \times 0.33} = 0.165$$

$$I_m^* = \frac{I_0 \sin \phi_0}{\sqrt{1 - \cos^2 \phi_0}}$$

$$= \frac{0.165}{\sqrt{1 - 0.33^2}} = 0.471 \text{ A}$$

$$= \frac{0.165}{\sqrt{1 - \cos^2 \phi_0}} = 0.471 \text{ A}$$

Q2

$$N_1 = 600$$

$$N_2 = 150$$

$$R_1 = 0.25 \Omega$$

$$R_2 = 0.01 \Omega$$

$$X_1 = 1.05 \Omega$$

$$X_2 = 0.04 \Omega$$

$$(a) R_{eq} = ?$$

$$(b) X_{eq} = ?$$

$$(c) Z_{eq} = ?$$

$$(d) \phi_1 = ?$$

$$K_2 = \frac{N_2}{N_1} = \frac{150}{600} = \frac{1}{4}$$

Page No.: _____
Date: _____

$$(a) R_{e1} = R_L + \frac{R_2}{K_2} = 0.25 + \frac{0.01}{(1/4)^2} \\ = 0.41 \Omega$$

$$(b) X_{e1} = X_1 + \frac{X_2}{K_2} = 1.0 + \frac{0.64}{(1/4)^2} \\ = 1.64 \Omega$$

$$(c) Z_{e1} = \sqrt{R_{e1}^2 + X_{e1}^2} \\ = \sqrt{(0.41)^2 + (1.64)^2} \\ = \sqrt{(0.16) + (2.68)} = 1.68$$

$$(d) \phi_1 = \tan^{-1} \left(\frac{R_{e1}}{X_{e1}} \right)$$

or

$$\tan^{-1} \left(\frac{X_{e1}}{R_{e1}} \right)$$