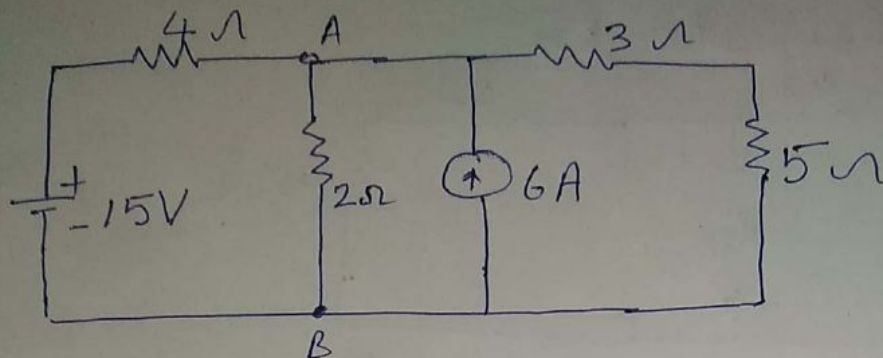


Tutorial sheet No 3


1)



$I_{2\Omega}$?
Using Thevenin's
Theorem.

Step 1) Load = 2Ω

Step 2)

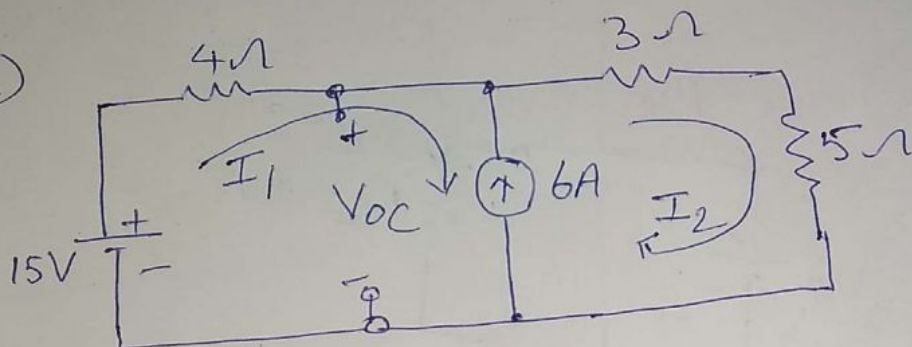

Step 3) Find $V_{oc} = V_{th}$

$$I_2 - I_1 = 6 \quad \text{or} \quad -I_1 + I_2 = 6 \quad \text{--- (1)}$$

KVL in mesh (1)

$$15 - 4I_1 - V_{oc} = 0$$

$$V_{oc} = 15 - 4I_1 \quad \text{--- (2)}$$

KVL in mesh (2)

$$-3I_2 - 5I_2 + V_{oc} = 0$$

$$V_{oc} = 8I_2 \quad \text{--- (3)}$$

From eqn (1) and (3)

$$15 - 4I_1 = 8I_2$$


$$-4I_1 - 8I_2 = -15 \quad \text{--- (4)}$$

$$I_1 = -2.75 \text{ A}, \quad I_2 = 3.25 \text{ A}$$

$$V_{oc} = 8 \times 3.25 \\ = 26 \text{ V}$$


$$V_{th} = 26 \text{ V}$$

Step 4) Calculate R_{th}

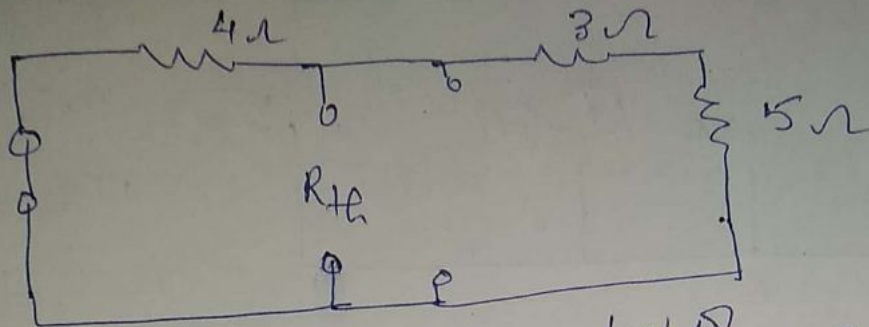

$$R_{th} = 4 \parallel 8 = \frac{4 \times 8}{12} = 2.67 \Omega$$


Step 5)

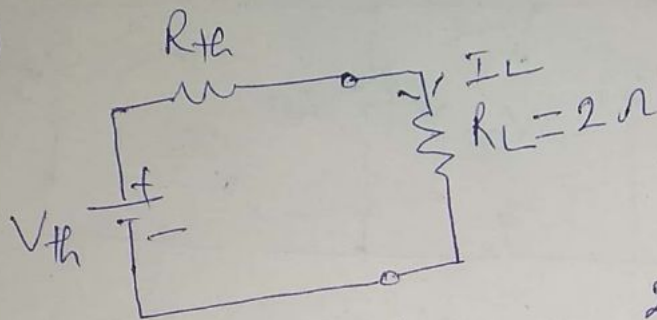

$$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{26}{2.67 + 2} = 5.57 A$$

Ans


2)

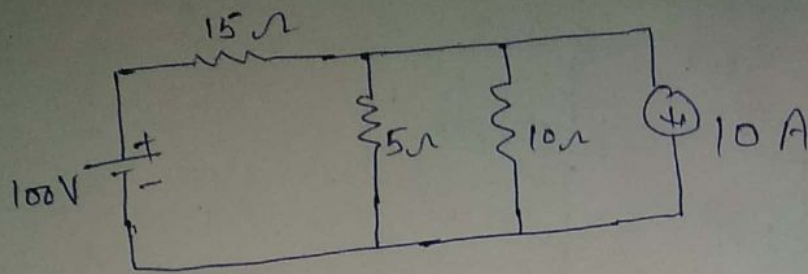

$I_{5\Omega}$ using
Thevenin's Theorem

Step 1) Load = 5Ω

Step 2) Remove 5Ω

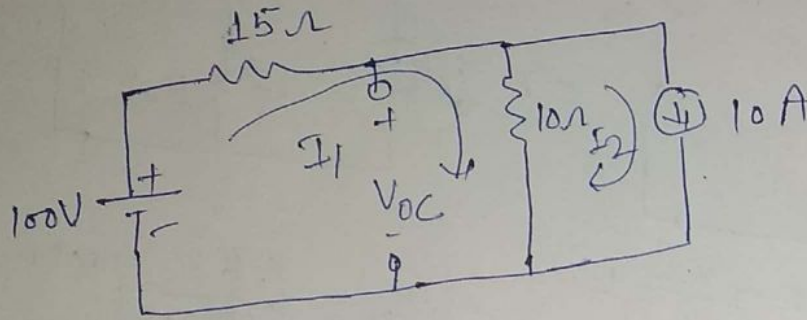

Step 3) Calculate V_{oc}

$$I_2 = 10 \text{ A}$$

$$100 - 15I_1 - 10(I_1 - I_2) = 0$$

$$25I_1 - 10I_2 = 100$$

$$25I_1 = 100 + 10I_2$$

$$= 100 + 10 \times 10 = 200$$

$$I_1 = 8 \text{ A}$$

$$100 - 15I_1 - V_{oc} = 0$$


$$\begin{aligned} V_{oc} &= 100 - 15I_1 \\ &= 100 - 15 \times 8 \\ &= -20 \text{ V} \end{aligned}$$

$$V_{th} = -20 \text{ V}$$

Step 4) Calculate R_{th}

$$R_{th} = 15 \parallel 10$$

$$= \frac{150}{25} = 6 \Omega$$

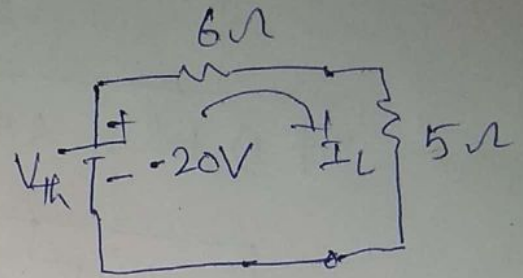


$$\begin{aligned} I_L &= \frac{V_{th}}{R_{th} + R_L} \\ &= \frac{-20}{6 + 5} \end{aligned}$$

$$= -\frac{20}{11}$$


$$= -1.82 \text{ A}$$

$= 1.82 \text{ A}$ from
bottom to top



Ans

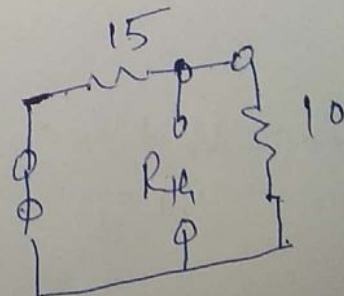

3(b)

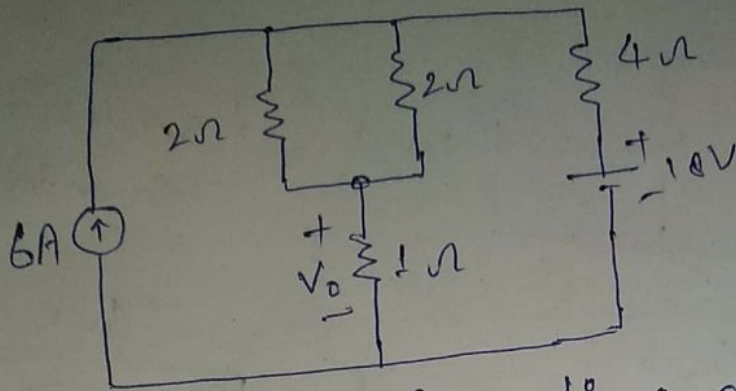

Step 1) When 6A is acting alone

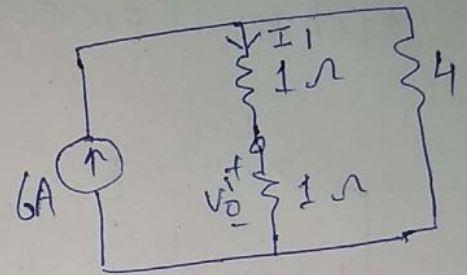
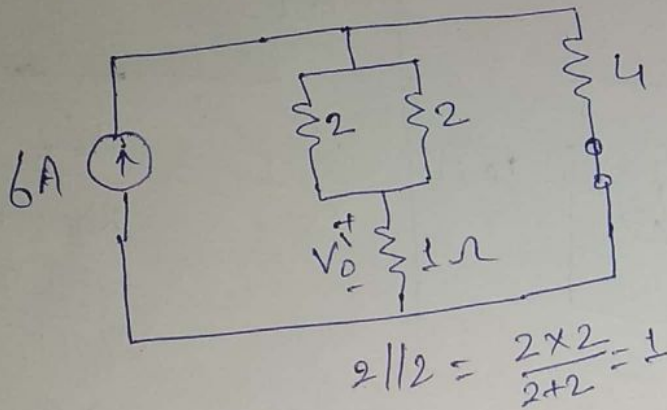


$$I_1 = \left[\frac{6}{4 + (1+1)} \right] \times 4$$

$$= \frac{6 \times 4}{6} = 4A$$

$$V_o' = 4 \times 1 = 4V - \textcircled{1}$$

Step 2) When 18V is acting alone.

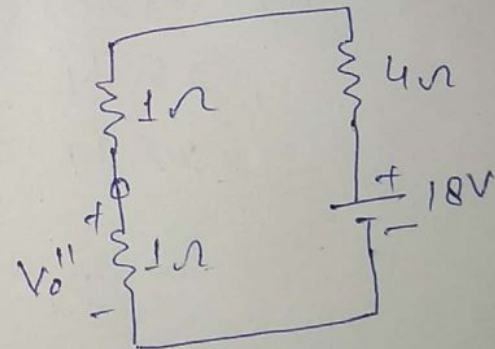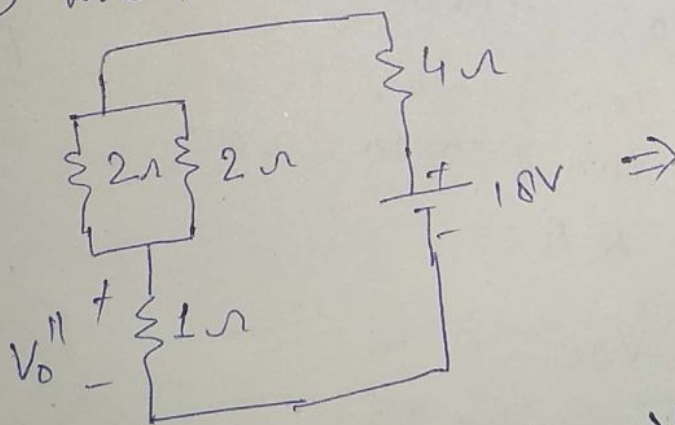

$$V_o'' = \left[\frac{18}{4 + (1+1)} \right] \times 1$$


$$= \frac{18}{6} = 3V$$

Step 3)


$$V_o = V_o' + V_o''$$

$$= 4 + 3 = 7V \text{ Ans}$$

4)

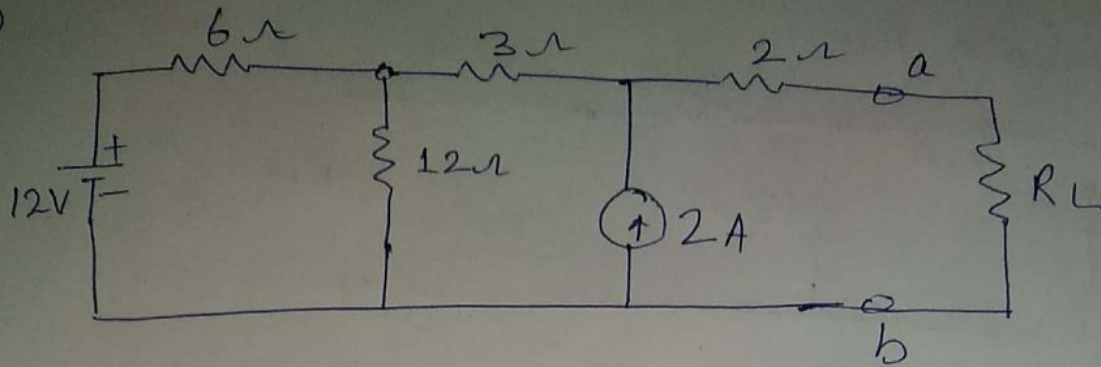

Step 1)

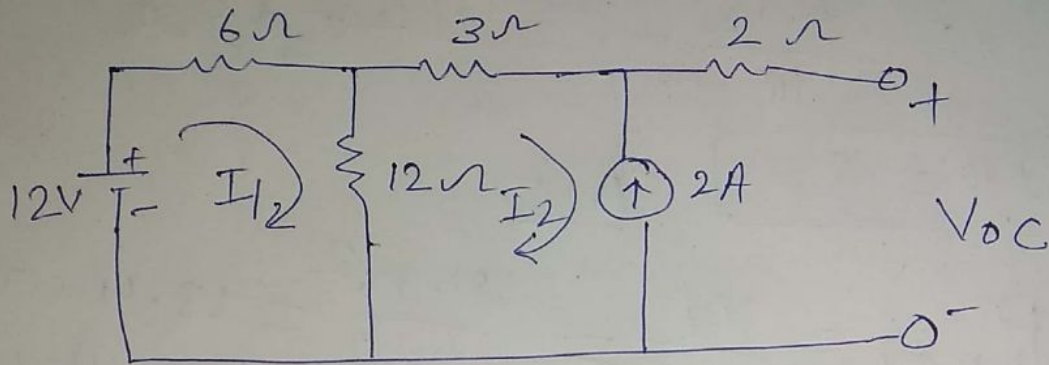Step 2) calculate V_{OC}

$$I_2 = -2A$$

KVL in mesh ①

$$12 - 6I_1 - 12(I_1 - I_2) = 0$$

$$18I_1 - 12I_2 = 12$$

$$18I_1 = 12 + 12I_2$$

$$= 12 + 12 \times (-2)$$

$$= 12 - 24 = -12$$

$$I_1 = \frac{-12}{18} = -0.67A$$

Apply KVL to get V_{OC}


$$-3I_2 - 0 \times 2 - V_{OC} - 12(I_2 - I_1) = 0$$

$$V_{OC} = -3I_2 - 12(I_2 - I_1)$$

$$= +12I_1 - 15I_2 = 12(-0.67) - 15 \times (-2)$$

$$= 21.96V$$

Step 3)
calculate R_{th}

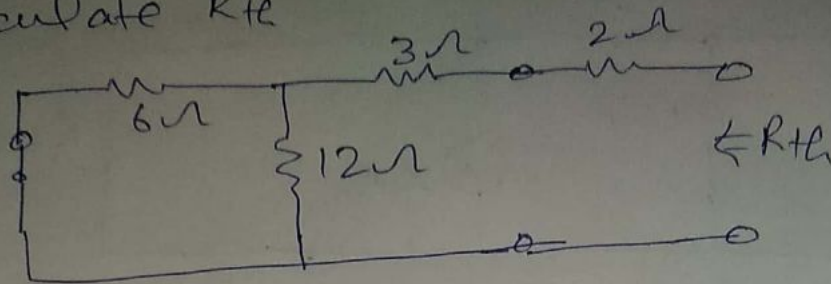

$$R_{th} = 6 \parallel 12 + 5$$


$$= \frac{6 \times 12}{18} + 5 = 4 + 5 = 9 \Omega$$

$$\boxed{R_{th} = 9 \Omega} \quad \text{Ans}$$


$$P_{L \max} = \frac{V_{th}^2}{4R_{th}} = \frac{21.96^2}{4 \times 9} = 13.4 \text{ watt}$$

Ans

⑤

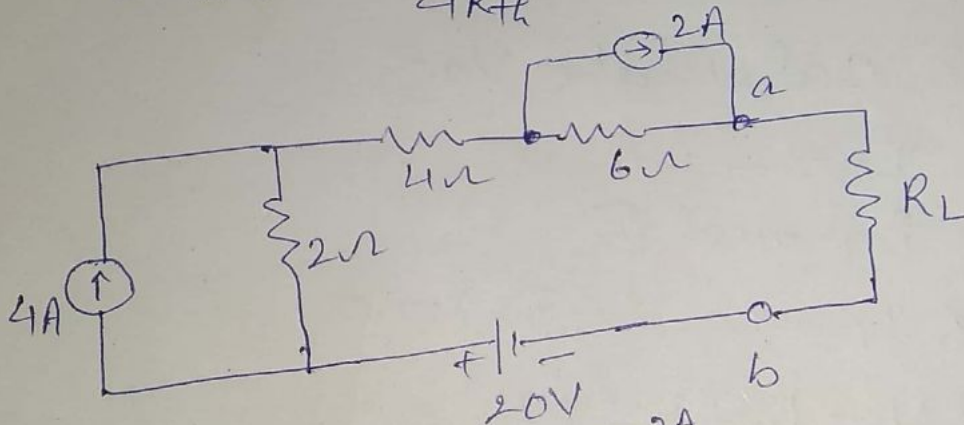

Step 1)

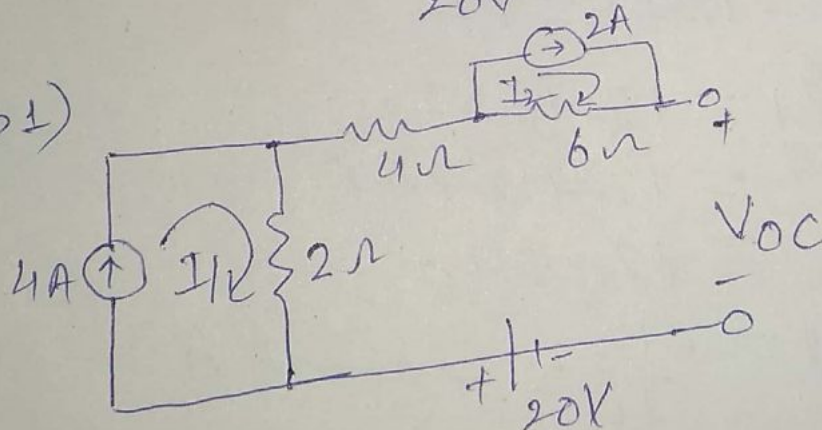

$$I_1 = 4 \text{ A}$$

$$I_2 = 2 \text{ A}$$

Apply KVL to get V_{OC}


$$-4 \times 0 - 6(-I_2) - V_{OC} + 20 - 2(-I_1) = 0$$

$$6I_2 + 20 + 2I_1 = V_{OC}$$

$$\begin{aligned}
 V_{OC} &= 20 + 2 \times 4 + 6 \times 2 \\
 &= 20 + 8 + 12 \\
 &= 40V
 \end{aligned}$$

$$V_{th} = 40V$$

Step 2) calculate R_{th}

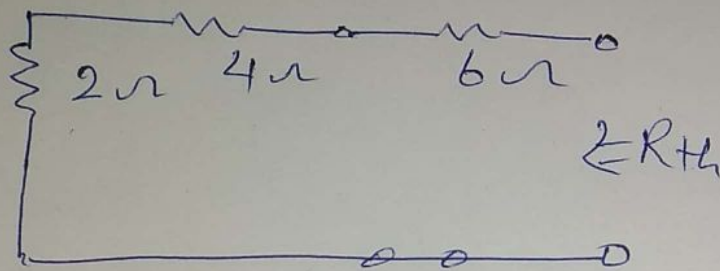

$$R_{th} = 2 + 4 + 6 = 12 \Omega$$

(a)

A circuit diagram showing a DC voltage source V_{th} in series with a resistor R_{th} and a load resistor R_L . The current flowing through the circuit is labeled I_L .

$$\begin{aligned}
 I_L &= \frac{V_{th}}{R_{th} + R_L} = \frac{40}{12 + 8} \\
 &= 2A \quad \underline{\text{Ans}}
 \end{aligned}$$

(b) $R_L = R_{th} = 12 \Omega \quad \underline{\text{Ans}}$

(c) $P_{L(max)} = \frac{V_{th}^2}{4R_{th}} = \frac{40^2}{4 \times 12} = 33.33 \text{ watt} \quad \underline{\text{Ans}}$

(d) $P_L = I_L^2 R_L = 2^2 \times 8 = 4 \times 8 = 32 \text{ watt} \quad \underline{\text{Ans}}$