

## Department of Electrical Engineering

EEE-1001  
Electrical Engineering

Session:2017-18  
Even semester

Tutorial sheet : 6  
Module II

1. Three loads, each of resistance 30 ohm, are connected in star to a 415 V, 3-phase supply. Determine (a) the system phase voltage, (b) the phase current and (c) the line current.  
**[Ans: 240 V, 8 A, 8 A]**
2. A star-connected load consists of three identical coils each of resistance  $30\Omega$  and inductance 127.3 mH. If the line current is 5.08 A, calculate the line voltage if the supply frequency is 50 Hz.  
**[Ans: 440 V]**
3. Three identical coils each of resistance  $30\Omega$  and inductance 127.3 mH are connected in delta to a 440 V, 50 Hz, 3-phase supply. Determine (a) the phase current, and (b) the line current.  
**[Ans: 8.8 A, 15.24 A]**
4. A balanced star-connected load of  $(4 + j3)\Omega$  per phase is connected to a 3-phase, 415 V, 50 Hz supply. Find (a) line current (b) the power factor (c) the power (b) the reactive volt-amperes and (e) the total voltamperes.  
**[Ans: 47.92A; 0.8 lagging; 27.56 kW; 20.67 kVAR; 34.4kVA]**
5. Three identical coils, each of resistance  $10\Omega$  and inductance 42 mH are connected (a) in star and (b) in delta to a 415 V, 50 Hz, 3-phase supply. Determine the total power dissipated in each case.  
**[Ans: 6.3 kW, 18.87 kW]**
6. Each arm of delta connected load has a resistance of  $25\Omega$ , an inductance of 0.15 H, and a capacitance of  $120\mu\text{F}$  in series. The load is connected across a 400 V, 50 Hz, 3-phase supply. Determine the line current, active power and reactive volt-amperes.  
**[Ans: 21.38 A, 11.43 kW, 9.42 kVAR]**
7. Three similar resistors connected in star draw a line current of 5 A from 400 V, 3-phase mains. To what value should the line voltage be changed to obtain the same line current with resistors connected in delta?  
**[Ans: 133.33 V]**